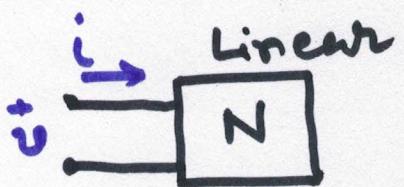


Impedance



Complex freq.
 $= \sigma + j\omega$

voltage of the form e^{st}


$$\frac{v}{i} = \text{Constant}$$

$Z(s)$ = Impedance



$$v = iR$$

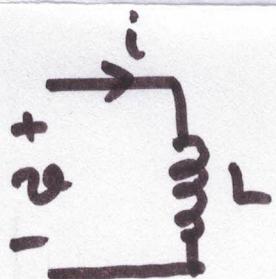
$$\frac{v}{i} = R \quad [\text{independent of } s]$$



$$v = L \frac{di}{dt} \quad i = e^{st} \quad (2)$$

$$v = sL e^{st}$$
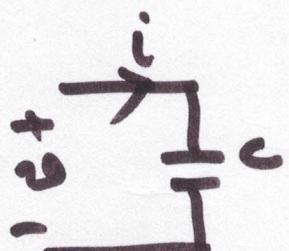
$$\frac{v}{e^{st}} = sL \Rightarrow \frac{v}{i} = sL = Z_L(s)$$



$$i = C \frac{dv}{dt} ; \quad v = e^{st}$$

$$\frac{v}{i} = \frac{1}{sC} = Z_C(s)$$

$$\text{Admittance} = \frac{1}{\text{Impedance}}$$

#1.

$$Z(s) = R + sL + \frac{1}{sC}.$$

#2.

$$Z(s) = R + \frac{1}{sL + \frac{1}{sC}}$$

$$= R + \frac{sL}{s^2LC + 1}$$

| | |
|-----------------------------------|----------------|
| $\frac{d}{dt} \rightarrow s$ | $v = 6e^{-2t}$ |
| $\int dt \rightarrow \frac{1}{s}$ | |

Phase.

(4)


Let F be a periodic signal, and T be its period i.e. $F(t+T) = F(t)$ for all t . Then the phase of F at any argument t is

$$\Phi(t) = 2\pi \left[\frac{t-t_0}{T} \right]$$


$[\cdot]$ → Represents the fractional part of a real m.

$t_0 \rightarrow$ beginning of a cycle.
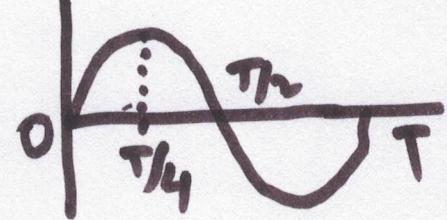
$$\Phi(t) = \frac{2\pi}{T} \left[\frac{\tau_{1/4} - 0}{T} \right]$$


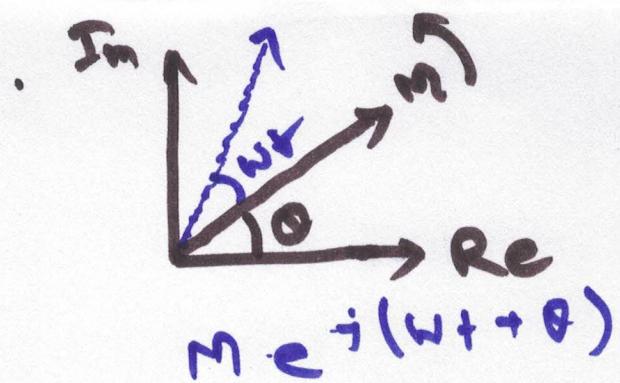
$$= 2\pi \left[\frac{\frac{T}{4}}{T} \right] = \frac{\pi}{2}.$$



$$\bar{M} = M e^{-j\theta} = M \angle \theta$$

* Phasor Let $v(t) = V_m \cos(\omega t + \theta)$

$$e^{st} = e^{(s+ja)t}$$

$$= e^{js\omega t}$$

$$= \operatorname{Re} [V_m e^{j(\omega t + \theta)}]$$

$$= \operatorname{Re} [\sqrt{2} V e^{j(\omega t + \theta)}$$

(RMS voltage)

Identifying quantity = $\operatorname{Re} [(v e^{j\theta}) (\sqrt{2} e^{j\omega t})]$

(phasor)

Representation of voltage $v(t)$

$$\bar{V} = V e^{j\theta}$$




$$\bar{I} = I_0 e^{j\alpha}$$

$$i(t) = R C [I_0 e^{j\alpha} \sqrt{2} e^{j\omega t}]$$
$$= \sqrt{2} I_0 \cos(\omega t + \alpha)$$

- (i) $i_1 = 10\sqrt{2} \cos \omega t \rightarrow \bar{i}_1 = 10 e^{j0} = 10 \angle 0^\circ$
- (ii) $i_2 = 10 \cos(\omega t + \frac{\pi}{6}) \rightarrow \bar{i}_2 = \frac{10}{\sqrt{2}} e^{j\frac{\pi}{6}}$
- (iii) $v_1(t) = 20\sqrt{2} \sin(\omega t + \frac{\pi}{6})$
 $= 20\sqrt{2} \cos(\omega t + \frac{\pi}{6} - \frac{\pi}{2})$
 $= 20\sqrt{2} \cos(\omega t - \frac{\pi}{3})$
 $\bar{v}_1 = 20 e^{-j\frac{\pi}{3}}$

(9)

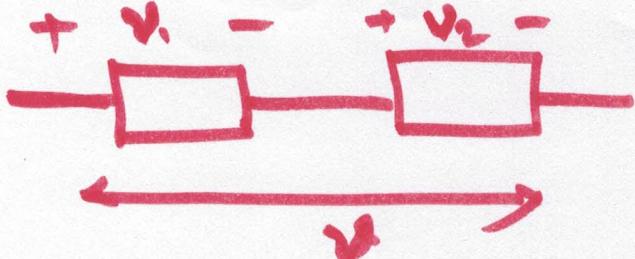

$$v_1 = 150\sqrt{2} \cos(100\pi t - \frac{\pi}{6})$$

$$v_2 = 200\sqrt{2} \cos(100\pi t + \frac{\pi}{3})$$

$$v = ?$$

① Graphical

$$\bar{v}_1 = 150 e^{-j\frac{\pi}{6}}$$

$$\bar{v}_2 = 200 e^{j\frac{\pi}{3}}$$

$$\Rightarrow \bar{v}_{\text{R}} = v_R < \theta$$

$$v = \sqrt{2} v_R \cos(\omega t + \theta)$$

② Analytical

(10)



$$\bar{v}_1 = 150 e^{-j\frac{\pi}{6}} = 130 - j75$$

$$\bar{v}_2 = 200 e^{j\frac{\pi}{3}} = 100 + j173$$

$$\bar{v}_1 + \bar{v}_2 = 1230 + j98$$

$$\bar{v} = 250 \angle 23.1^\circ$$
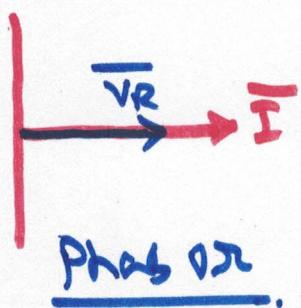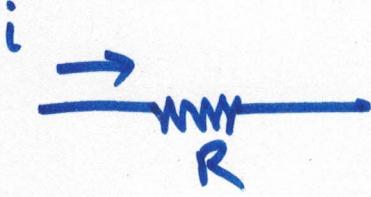
$$v = 250\sqrt{2} \cos(100\pi t + 23.1^\circ)$$




$$i = \sqrt{2} I \cos \omega t . \quad (11)$$

$$\bar{I} = I e^{j0^\circ} = I \angle 0^\circ$$

$$\bar{V}_R = \bar{I} R = V_R \angle 0^\circ$$

$$v_R = \sqrt{2} I R \cos \omega t$$
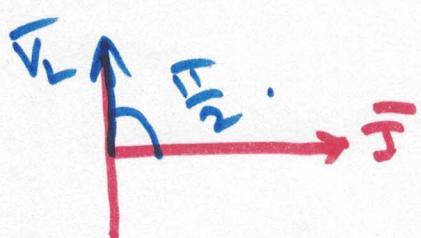
$$\frac{\bar{V}_R}{\bar{I}} = R = R \angle 0^\circ$$



$$i = \sqrt{2} I \cos \omega t . \quad (12)$$

$$\bar{I} = I \angle 0^\circ$$

$$v = L \frac{di}{dt}$$

$$= -\omega L \sqrt{2} I \sin \omega t$$


$$= \sqrt{2} \omega L I \cos \left(\omega t + \frac{\pi}{2} \right)$$

$$\bar{V}_L = \omega L I \angle \frac{\pi}{2} .$$

$$= V_L \angle \frac{\pi}{2} .$$

$$\frac{\bar{V}_L}{\bar{I}} = \omega L \angle \frac{\pi}{2} = Z_L \text{ (Impedance)}$$

$$= j \omega L$$

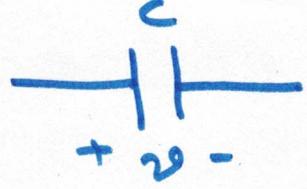

$$v = \sqrt{2} V \cos \omega t \rightarrow \bar{v} = V \angle 0^\circ$$

$$i = C \frac{dv}{dt}$$

$$= -\sqrt{2} \omega C V \sin \omega t$$

$$\text{---} \uparrow \frac{\pi}{2} \rightarrow \bar{v} \quad i = \sqrt{2} \omega C V \cos \left(\omega t + \frac{\pi}{2} \right)$$

$$\bar{i}_c = \omega C V \angle \frac{\pi}{2}.$$

$$\frac{\bar{V}}{\bar{i}_c} = \frac{1}{\omega C \angle \frac{\pi}{2}} = \frac{1}{j \omega C} \\ = Z_C$$

(Not a phasor)

$$\overline{I_R} \rightarrow \text{---} \uparrow \frac{\pi}{2} \rightarrow \bar{v}_R - \\ + \bar{v}_R -$$

$$\bar{v}_R = R \bar{I}_R$$

$$\bar{I}_R = \frac{\bar{v}_R}{R} \\ = G \bar{v}_R$$

$$\sqrt{2} K \cos(\omega t + \theta)$$

$$\overline{I_L} \rightarrow \text{---} \uparrow \bar{v}_L -$$

$$\bar{v}_L = j \omega L \bar{I}_L$$

$$\bar{I}_L = \frac{\bar{v}_L}{j \omega L}$$

$$Z_L = j \omega L$$

$$Y_L = \frac{1}{j \omega L}$$

$$\overline{I_C} \rightarrow \text{---} \uparrow \bar{v}_C -$$

$$\bar{v}_C = \frac{1}{j \omega C} \bar{I}_C$$

$$\bar{I}_C = j \omega C \bar{v}_C$$

$$Z_C = \frac{1}{j \omega C}$$

$$Y_C = j \omega C.$$

when impedance is purely imaginary

(15)

$$Z_L = j\omega L = jX_L$$


$X_L = \omega L$ = Reactance.

$$Y_C = j\omega C = jB_C$$

$B_C = \omega C$ = Susceptance of C.

$$Z_C = j \left(-\frac{1}{\omega C} \right) = jX_C$$

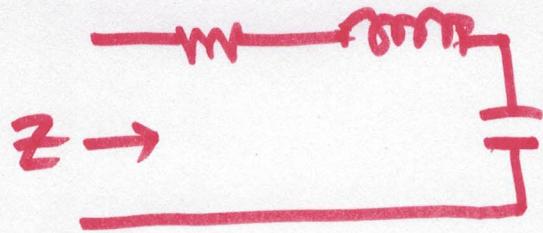$X_C = -\frac{1}{\omega C}$ = Reactance of C




$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j \left(\omega L - \frac{1}{\omega C} \right)$$

Resistive point

Reactive point

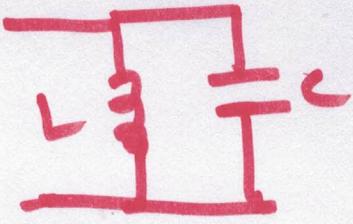

$$Z = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{j\omega L}{1 - \omega^2 LC}$$

$$\omega^2 LC = 1$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Resonant condition

Impedance $\rightarrow \infty$

KVLKCL

(17)


$$\sum_i v_i = 0$$

$$\sum_j i_j = 0$$

$$Re \sum_i \sqrt{2} v_i e^{j\theta} e^{j\omega t} = 0$$

$$\sum_i \bar{v}_i = 0$$

$$\sum_j \bar{i}_j = 0$$

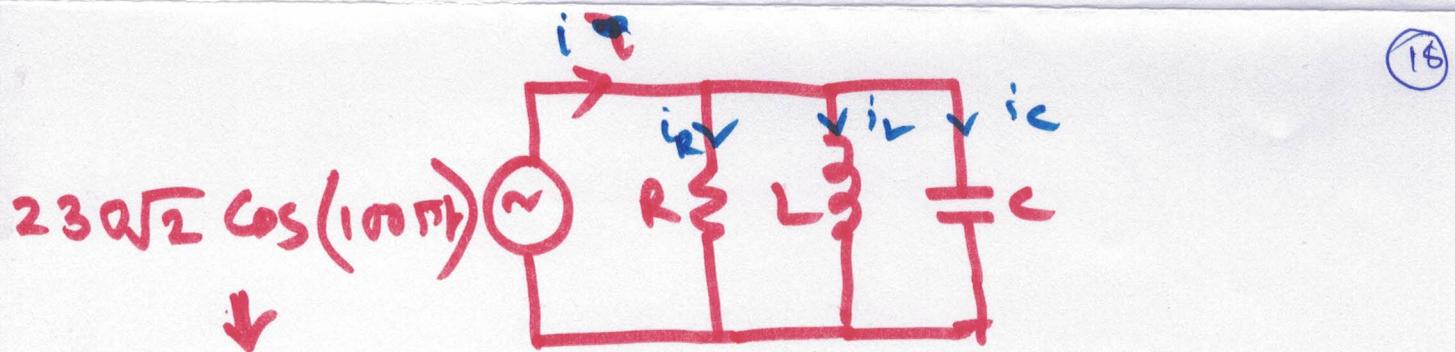

$$230 \angle 0^\circ$$


$$\bar{i}_R = \frac{230}{R} \angle 0^\circ$$

$$\bar{i}_L = \frac{230}{\omega L} \angle -\frac{\pi}{2}$$

$$\bar{i}_C = \frac{230}{\frac{1}{\omega C}} \angle \frac{\pi}{2}$$

$$\bar{i} = \bar{i}_R + \bar{i}_L + \bar{i}_C$$

$$i =$$

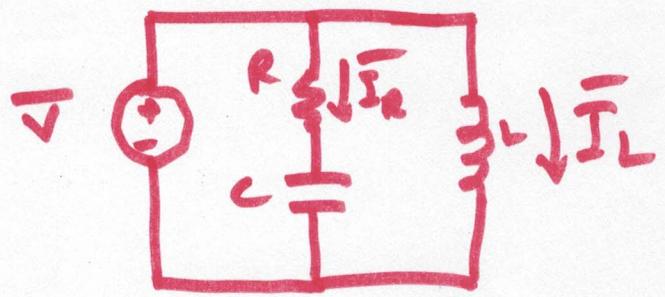

$$R = 2 \Omega, L = 0.2 H$$



$$i_R = 10\sqrt{2} \cos(10t + 45^\circ)$$

- 19(i) Show \bar{i}_R & \bar{v}_R in a phasor diagram.
- (ii) Show the direction of \bar{v}_c
- (iii) If the voltage phasor $\bar{V} = V \angle 0^\circ$, $v(t) =$

$$\bar{i}_R = 10 \angle 45^\circ$$

$$\bar{v}_R = 20 \angle 45^\circ$$
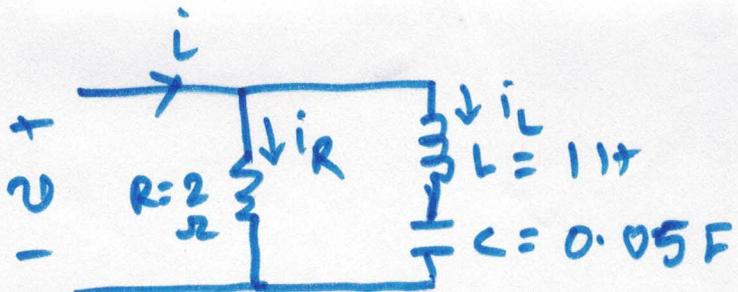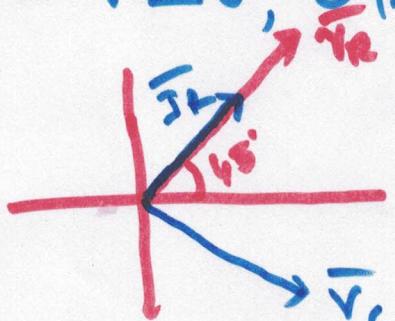
$$\bar{v}_c = \frac{\bar{i}_R}{j\omega C} = \frac{\bar{i}_R}{\omega C} \angle -\frac{\pi}{2}$$





$$v(t) = 5\sqrt{2} \cos 55t$$

$$v_c = ?$$

Complete Phasor Diagram.


Thevenin & Norton:-

①

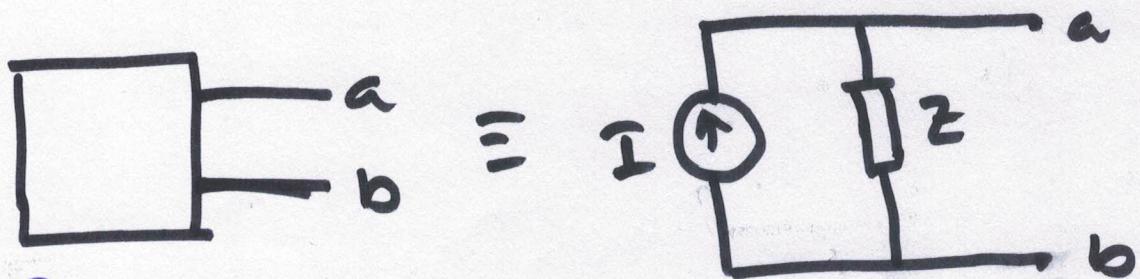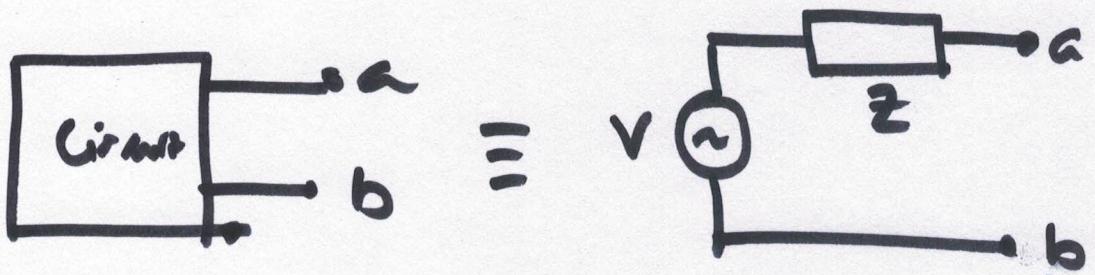

- ① Find V_{OC}
- ② Find I_{SC} . $\Rightarrow Z = \frac{V_{OC}}{I_{SC}}$

②

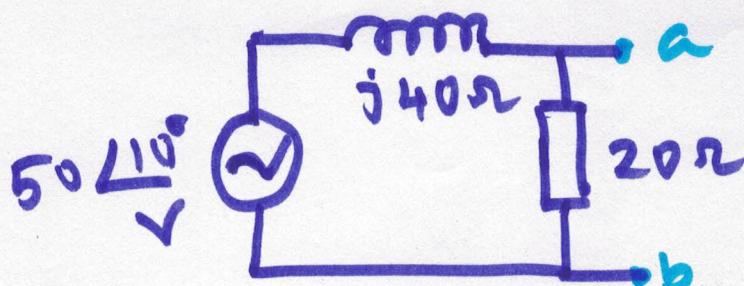

By killing source:-


$$\text{Diagram shows the circuit with the dependent voltage source removed (killed).}$$

$$Z = Z_{ab} = \frac{j40 \cdot 20}{20 + j40} = 16 + j8$$


$$V_{OC} = V_{ab} = \frac{20}{20 + j40} 50 \angle 10^\circ$$

$$V_{ab} = \frac{1}{\sqrt{5}} \angle 63.4^\circ \quad 50 \angle 10^\circ$$

$$V_{ab} = 22.3 \angle -53.4^\circ$$

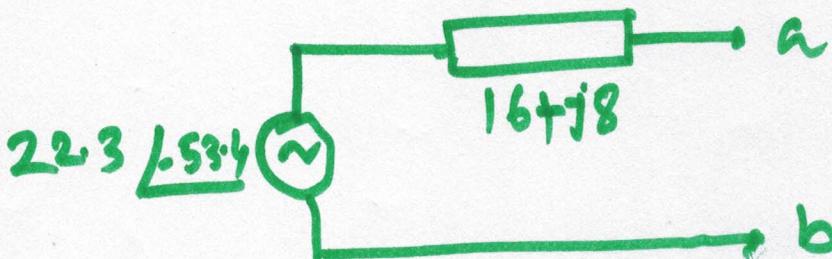


Thevenin Equivalent

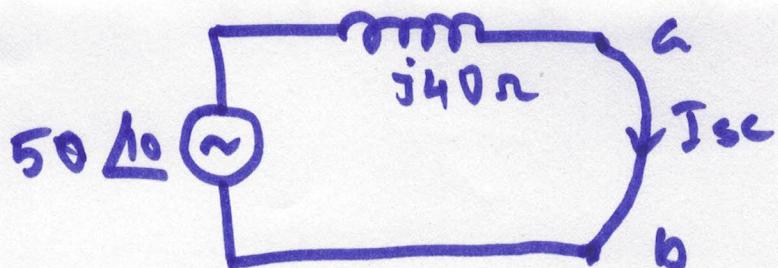


$$I_{sc} = \frac{50 \angle 10^\circ}{j40} = \frac{50 \angle 10^\circ}{40 \angle 90^\circ}$$

$$= 1.25 \angle -80^\circ$$

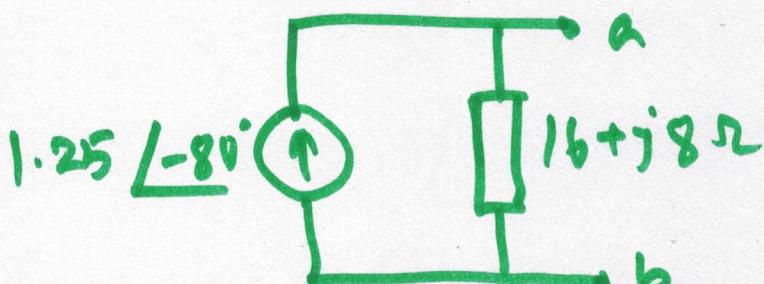

Norton's Equivalent

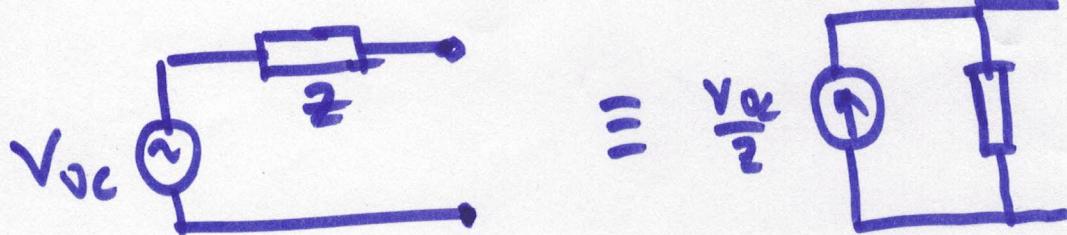

$$\begin{aligned}\frac{V_{OC}}{Z} &= \frac{22.3 \angle -53.4^\circ}{16 + j8} \\ &= \frac{22.3 \angle -53.4^\circ}{17.89 \angle 26.6^\circ} \\ &= 1.25 \angle -80^\circ\end{aligned}$$

(By Source Transformation)